# Powering the PUMA Dec14-08

Dr. Greg Luecke – Client/Advisor Matt Bogenschultz Alex Grieve Nhat Pham Seth Taylor Zeyu Zhang

# Background

- PUMA robot
  - Lightweight
  - 6 moveable joints
  - Precise, repeatable movement
- Used in research
  - Dr. Luecke
  - Haptics & feedback
  - Kinematics



# Problem

#### Original controller

- Does not provide torque control
- Damaged beyond reasonable repair
- Client needs a new controller
  - Torque control for all 6 joints
  - Control through C code
  - Utilize existing H-bridge design



# The Solution

- Over 400 wire connections, 20 PCBs
- 2500 lines of code
- All packed into a 2.3 ft<sup>3</sup> enclosure





# **Torque Control**

- $\tau = k_t * I$ 
  - $k_t = motor torque constant$
  - I = current through motor
- Can control average current with PWM signal
  - So, torque can be controlled







# H-Bridge

- Allows bi-directional rotation of the motor
  - H-Bridge allows a path for current across the motor
- Back EMF's
  - Caused voltage polarity changes, solved with diodes







### **PWM** Control

- PWM signals the H-Bridge to open and close
  - Duty cycle proportional to input



### PWM

			V				
			• • • • • • • •				
		· · · — — — — — — — — — — — — — — — — —					
····>100	C Pot						
····>/***	7 7 <del>7 7</del> 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7		· - · · · · · ·				
		$\cdots$	· • • • • • • • • • • • • • • • • • • •				
	· • · · · ·	· · · · //			110		
		· · · · <· T	·>N · · · ·		02		
	·   · · · ·   · ·U1	🔊	× 🛣 · ·   ·	1			
		<b>1</b> · · · · Y	· 🔂 · ·   ·	VCC.			
			🖵	RST	TUC		
L <b>RZ</b> .	RST OUT						
		· · ·   📥		DIS		. PWM C	output
	DIS						
				THE	. 61		
1::::::f:::		::: <b> </b> ♠		THR	55		
<b>.</b>	THR			THR	550		
· · · · · · · · · · · · · · · · · · ·				THR TRI	55 <b>C</b> N		
			· · · · · · · ·	THR TRI	555CN	· · · · · · · · · · · · · · · · · · ·	
			· · · · · · · · ·	THR TRI CON	555CN		
	THR 555 TRI CON		R3	THR TRI CON	55CN		
	THR 5550 TRI 000		R3	THR	555CN		
C1	THR 555 TRI 555 CON CON CON		R3 >100Ω	THR TRI GON GND	555CN		
C1	THR 555 TRI C2		R3 ≶100Ω	THR TRI GON GND	555CN		
C1		C3	R3 ≶100Ω	THR TRI CON GND	555CN		
C1 100nF == =	C2 GND 100nF		R3 ≶100Ω	THR . TRI . GON . GND.	555CN		
C1 100nF == =	C2 GND.	C3 (00nF	R3 ≶100Ω	THR . TRI . GON . GND.	555CN		
C1 100nF =	C2 GND	.C3 (00nF	R3 ≶100Ω	THR	555CN		
C1 100nF =		.C3 (00nF	R3 ≶100Ω	THR TRI CON GND	555CN		
C1 100nF ======	C2 GND	.C3 (00nF	R3 ≥100Ω — Input	THR	555CN		
C1 100nF == =	C2 GND.	C3 (00nF	R3 ≥100Ω — Input	THR	555CN		
C1 100nF == =	C2 GND.	C3 (00nF	R3 ≶100Ω — Input	THR TRI GON GND	555CN		
C1 100nF =		.C3 (00nF	R3 ≶100Ω — Input	THR TRI GON GND	555CN		



### Motenc-Lite

- Industrial grade, 4-axis motion control and data acquisition card
- Provides interface to hardware/circuits
  - PWM, H-Bridge, Motors, Encoders, Pots
- Uses PCI interface
  - Controllable through code
  - Meets functional requirement
- 8 Channel DAC, ± 10 V
  - Use analog outputs to control PWM circuit
- Built-in hardware for encoders and potentiometers
  - Encoders = relative position
  - Pots = absolute position

# C Code

#### Collection of functions (library)

- Search for and memory map the MOTENC cards
- Abstracts away messy details of writing DAC, reading encoders/pots, etc.
- Error checking prevents dangerous states

#### Safe shutdown

- Signal catching unexpected crash/shutdown
- Turns off all outputs, applies brake
- Skeleton file
- Configuration file
  - Individual tuning of different PUMAs



# **Power Delivery**

- Six motors in parallel to power supply
  - Sharing current limits available power to joints
- Dedicated power modules
  - Isolates each motor
- Auxiliary circuit power
  - For remaining active devices
  - Breakers and relays protect controller from spikes/surges





# Safety Circuit

- Provides protection for PUMA and operators
  - Emergency stop
  - Motor on/off
  - Surge protection
  - Electromechanical brake indicator
    - Indicates PUMA in motion





### Electromagnetic Brake

- Locks lower three joints for safety
- Half H-Bridge w/ 100% duty
- Cruical that brake is applied:
  - Program crashes
  - E-Stop pressed



### Main Board

- > 100 connections
- Bypass capacitors
  - Smooth voltage across motors





# Test Plan

- Ensure that each subsystem works as designed
  - Test circuits individually
- Ensure that subsystems work in circuit
  - Combine circuits one at a time
- Ensure code works with robot
  - Full system test

# Demo Video

http://dec1408.ece.iastate.edu/media/videos/demo.mp4

# Enclosure

- Protect our PCBs and power supplies
- Need fans for air-flow cooling
  - H-Bridge produces lots of heat
- Chassis ground isolations



# **Additional Slides**

### Status Sub-circuit

- Electronic components fail over time
- Sub-circuit indicates which component has failed
  - Opto-isolators sense damaged components
  - Logic gates and LEDs provide visual cues
- Need to account for current transfer ratio (CTR)
  - Individually tuned RC circuit for each opto-isolator

